

ECE-593

FUNDAMENTALS OF PRE-SILICON VALIDATION

Final Project Report

**Implementation and Verification of Asynchronous FIFO using
both Class-based and UVM methodologies.**

Section-1

Team-1

Kumar Durga Manohar Karna

Mohammed Abbas Shaik

Nivedita Boyina

Nikhitha Vadnala

Contents:

- Introduction
- Design Specifications
- FIFO depth Calculations
- Resources
- GitHub link


Introduction:

An Asynchronous FIFO (First in first out) is a specialized type of FIFO buffer that allows data to be read and written in different clock domains. Unlike a synchronous FIFO, where the read and write operations are controlled by the same clock signal, an Asynchronous FIFO will have separate read and write clock domains, enabling data transfer between two independently clocked systems.

The Asynchronous FIFO acts as a bridge between the sender and receiver modules, providing a reliable and efficient means of transferring data across different clock domains. It prevents data loss or data corruption during the transfer process, even when the write and read clocks are completely asynchronous to each other.

The design of an Asynchronous FIFO involves several challenges, such as metastability handling, gray code pointers, and synchronization techniques. Metastability can arise when data is transferred across asynchronous clock domains, which leads to undefined logic states. Proper metastability handling techniques, such as synchronizers, ensure reliable data transfer across clock domain boundaries. Grey code pointers with the property of changing only one bit at a time, which reduces the metastability. It also tracks the read and write positions in the memory. Additionally, the design incorporates synchronization techniques to properly coordinate the data transfer between the asynchronous clock domains.

Design Specifications:

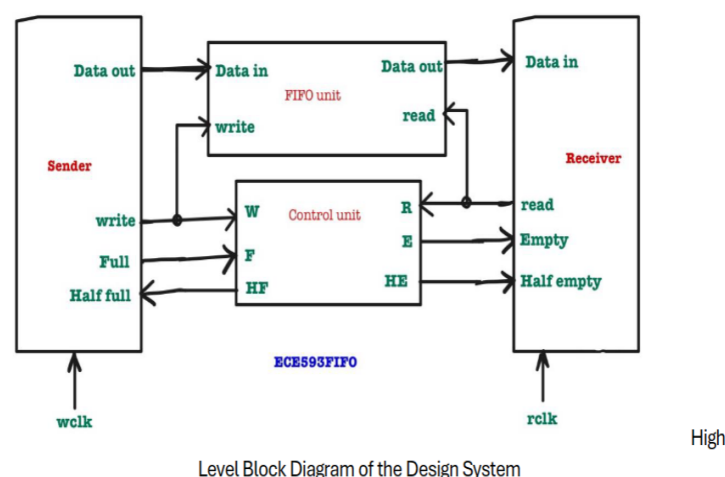

To understand the FIFO design, we need to understand how the FIFO pointers work. The write pointer always points to the next word to be written; therefore, on reset, both pointers are set to zero, which also happens to be the next FIFO word location to be written. On a FIFO-write operation, the memory location that is pointed to by the write pointer is written, and then the write pointer is incremented to point to the next location to be written.


Similarly, the read pointer always points to the current FIFO word to be read. On reset, both pointers are reset to zero, the FIFO is empty, and the read pointer is pointing to invalid data (because the FIFO is empty, and the empty flag is asserted). As soon as the first data word is written to the FIFO, the write pointer increments, the empty flag is cleared, and the read pointer that is still addressing the contents of the first FIFO memory word, immediately drives that first valid word onto the FIFO data output port, to be read by the receiver logic. The fact that the read pointer is always pointing to the next FIFO word to be read means that the receiver logic does not have to use two clock periods to read the data word. If the receiver first had to increment the read pointer before reading FIFO data word, the receiver would clock once to output the data word from the FIFO, and clock a second time to capture the data word into the receiver. That would be needlessly inefficient.

The FIFO is empty when the read and write pointers are both equal. This condition happens when both pointers are reset to zero during a reset operation, or when the read pointer catches up to the write pointer, having read the last word from the FIFO.

FIFO is full when the pointers are again equal, that is, when the write pointer has wrapped around and caught up to the read pointer. This is a problem. The FIFO is either empty or full when the pointers are equal, but which?

One design technique used to distinguish between full and empty is to add an extra bit to each pointer. When the write pointer increments past the final FIFO address, the write pointer will increment the unused MSB while setting the rest of the bits back to zero as shown in Figure 1 (the FIFO has wrapped and toggled the pointer MSB). The same is done with the read pointer. If the MSBs of the two pointers are different, it means that the write pointer has wrapped one more time than the read pointer. If the MSBs of the two pointers are the same, it means that both pointers have wrapped the same number of times.

 Using n -bit pointers where $(n-1)$ is the number of address bits required to access the entire FIFO memory buffer, the FIFO is empty when both pointers, including the MSBs are equal. And the FIFO is full when both pointers, except the MSBs are equal.



FIFO depth Calculations:

$f_A > f_B$ with idle cycles in both write and read.

Writing frequency = $f_A = 120\text{MHz}$.

Reading Frequency = $f_B = 50\text{MHz}$.

Burst Length = No. of data items to be transferred = 1024.

No. of idle cycles between two successive writes is = 4.

No. of idle cycles between two successive reads is = 2.

The no. of idle cycles between two successive writes is 4 clock cycle. It means that, after writing one data, module A is waiting for four clock cycle, to initiate the next write. So, it can be understood that for every five clock cycles, one data is written.

The no. of idle cycles between two successive reads is 2 clock cycles. It means that, after reading one data, module B is waiting for 2 clock cycles, to initiate the next read. So, it can be understood that for every three clock cycles, one data is read.

Time required to write one data item = $5 \times 1/120\text{ MHz} = 41.67\text{ ns} = 42\text{ ns}$

Time required to write all the data in the burst = $1024 * 42 \text{ ns.} = 43008 \text{ ns.}$

Time required to read one data item = $3 * (1/50) \text{ MHz} = 60 \text{ ns.}$

So, for every 60 ns, module B is going to read one data in the burst.

So, in a period of 43008 ns, 1024 no. of data items can be written.

The no. of data items can be read in a period of 43008 ns = $43008 \text{ ns} / 60 \text{ ns} = 717$

The remaining no. of bytes to be stored in the FIFO = $1024 - 717 = 307$.

So, the FIFO which has to be in this scenario must be capable of storing 307 data items.

So, the minimum depth of the FIFO should be 307.

Resources:

1. http://www.sunburst-design.com/papers/CummingsSNUG2002SJ_FIFO1.pdf
2. http://www.sunburst-design.com/papers/CummingsSNUG2002SJ_FIFO2.pdf
3. <https://hardwaregeeksblog.files.wordpress.com/2016/12/fifodepthcalculationmadeeasy2.pdf>
4. <https://ieeexplore.ieee.org/abstract/document/7237325>

GitHub link:

https://github.com/BNiVeDiTa29/ECE593s24_team_01_Async_FIFO